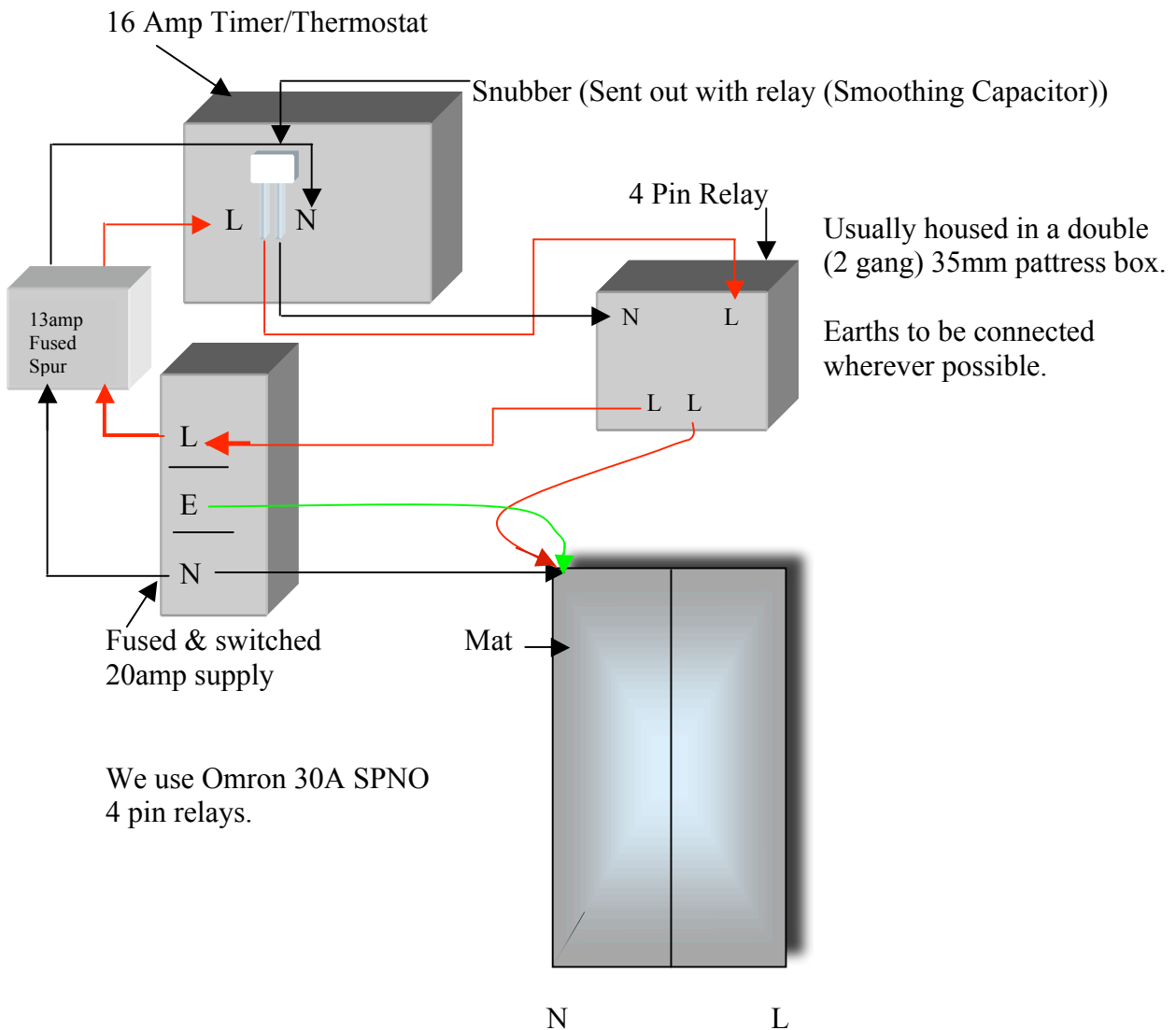


Wiring up a relay



When wiring to a relay always have the positive running directly to it and the negative & earth running to the supply.
The control is wired to the supply and relay.